Procedimiento:

1.- Realizar la reducción de la siguiente expresión booleana con las propiedades del algebra de Boole, dibujar la solución con simbología y una vez que tengas la solución comprobar con tablas la verdad y también comprobar con un PLD las ecuaciones resultantes.

Ej. Solución F(A,B,C,D) = AB + A'D' + BD' + A'B + CD'A + A'D + CD + A'B'C' = B + A' + C

Α	В	С	A'+B + C
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

```
1. \overline{XYZ} + \overline{Y}(XZ + X\overline{Z}) Solución: \overline{ABC} + \overline{B}(AC + A\overline{C}) = \overline{B}[A(C + \overline{C})] = \overline{ABC} + \overline{B}A = \overline{A} + \overline{B} + \overline{C} + \overline{B}A = \overline{A} + \overline{B} + \overline{C}
```

Α	В	С	OUTPUT
0	0	0	1
0	0	1	1
0	1	0	1

```
entity Prog1 is
    Port ( a : in STD_LOGIC;
        b : in STD_LOGIC;
        c : in STD_LOGIC;
        d : in STD_LOGIC;
        x : out STD_LOGIC;
        y : out STD_LOGIC);
end Prog1;

architecture Behavioral of Prog1 is

begin
x <= (a and b and c) not or (b not) and (a not and c or a and c not);
y<= (a not) or (b not) or (c not);
end Behavioral;</pre>
```

```
      0
      1
      1

      1
      0
      0

      1
      0
      1

      1
      1
      0

      1
      1
      1

      1
      1
      0
```

```
entity Progl is
Port (
a: in STD_LOGIC;
b: in STD_LOGIC;
c: in STD_LOGIC;
d: in STD_LOGIC;
x: out STD_LOGIC;
Y: out STD_LOGIC;
end Progl;

architecture Behavioral of Prog1 is
begin x <= (a and b and c) not or (b not) and (a not and c a and c not);
Y<= (a not) or ( (b not) or (c not);
end Behavioral;
```

$$\overline{(Z+\overline{X}\overline{Y})(\overline{Y+\omega})}$$

$$\overline{\left[C + \overline{A}\overline{B}\right]\left[\overline{B} + \overline{D}\right]} = \overline{\left[C + \overline{A} + \overline{B}\right]} + \overline{\left[\overline{B} + \overline{D}\right]} = \overline{\left[C + A + \overline{B}\right]} + \overline{\left[B + D\right]} =
= \overline{\left[C \cdot \overline{A} \cdot \overline{B}\right]} + \overline{\left[B + D\right]} = \overline{C}\overline{A}B + B + D = \mathbf{B} + \mathbf{D}$$

Α	В	С	D	OUT
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1

0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1

1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

```
entity Prog2 is
Port (a : in STD_LOGIC;
b : in STD_LOGIC;
c: in STD_LOGIC;
d : in STD_LOGIC;
X : out STD_LOGIC;
y : out STD_LOGIC);
end Prog2;
architecture Behavioral of Prog2 is
begin
x<= ((c or a not and b) and (b or d) not) not;
Y<= b or d;
end Behavioral;</pre>
```

3.

$$(\overline{X+Y}+Yzw)\overline{XY}$$

 $\overline{(\overline{A} + \overline{B} + BCD)}\overline{AB} = \overline{(\overline{A} + \overline{B} \cdot \overline{BCD})}[\overline{A} + \overline{B}] = [A\overline{B} + A\overline{C} + A\overline{D} + B\overline{C} + B\overline{D}][\overline{A} + \overline{B}] = \overline{ABC} + \overline{ABD} + A\overline{B} + A\overline{CB} + A\overline{DB} = \overline{ABC} + \overline{ABD} + A\overline{B} = \overline{ABC} + \overline{ABD} + A\overline{B}$

0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0

Α	В	С	D	OUT
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0

1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

entity Prog3 isPort (a: inb: in.ind: in0 0 0 0 0STD_LOGIC;STD
LOGIC;STD_LOGIC;STD
LOGICHSTD_LOGIC;STD_LOGIC);x:o
uty: outend Prog3;architecture
Behavioral of Prog3 isbeginx<= (((a or b) not or b and b and c and d))
notand (a and b) not;y<= a not and b and (c not or d not) or a and b not;and Behavioral.

Circuito 74LS21(AND 4 ENTRADAS)


X	Υ	z	w	SALIDA
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0


Circuito	Circuito 74LS00(NAND)				
X	Υ	SALIDA			
0	0	1			
0	1	1			
1	0	1			
1	1	0			

		Circ	uito 74L10	(NAND 3
X	Y	Z	SALIDA	S
0	0	0	1	D" D"
0	0	1	1	0" 0"
0	1	0	1	D'' D''
0	1	1	1	D''
1	0	0	1	0**
1	0	1	1	D" D"
1	1	0	1	D" D"
1	1	1	0	D" D" D"

Circuito 74L04(NOT)		
Х	SALIDA	
0	1	
1	0	


Circuito 74L86(XOR)					
X	Υ	SALIDA			
0	0	0			
0	1	1			
1	0	1			
1	1	0			

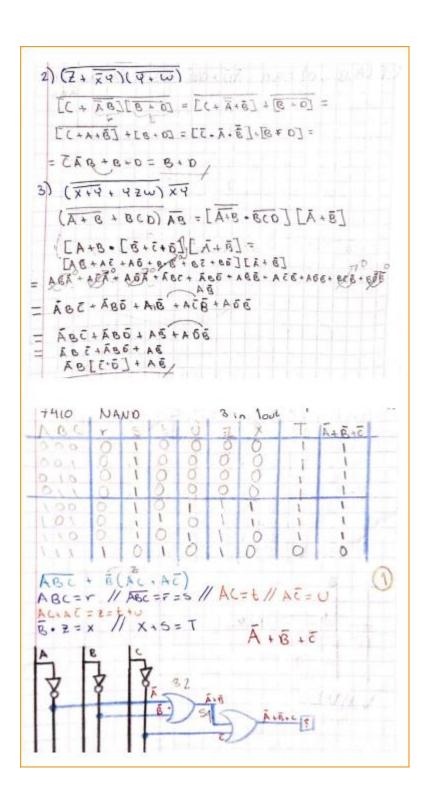

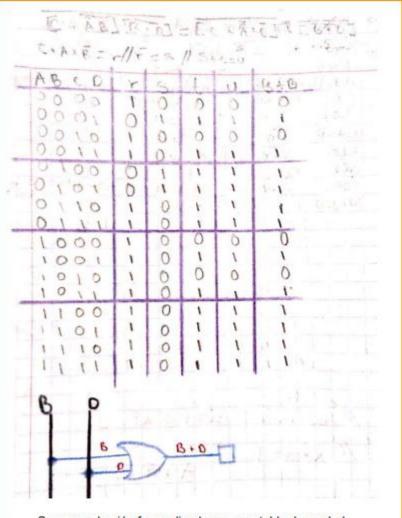

Su comprobación fue realizada con una tabla de verdad

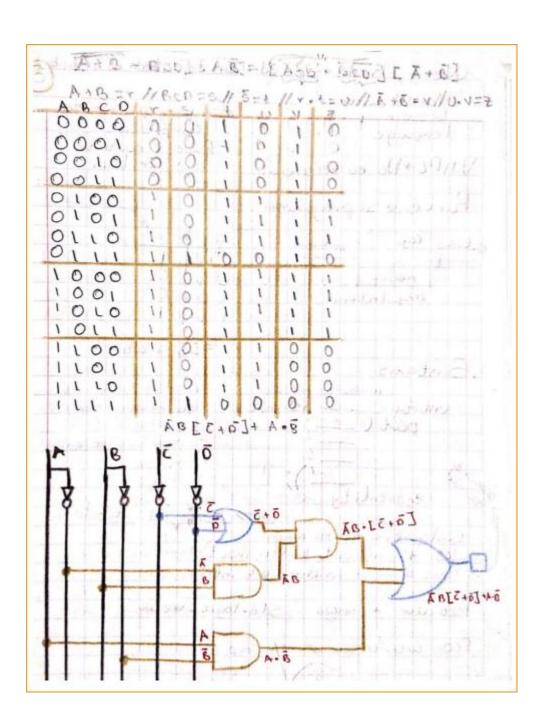Se realizaros los diagramas correspondientes de sus reducciones



4.- Documentar la practica con comentarios de cada una de las operaciones.

Operaciones del ejercicio 2

$$\frac{1)}{A8C} + \frac{8}{8}(AC + AE)$$

$$ABC + \frac{8}{8}(AC + AE)$$

$$ABC + \frac{8}{8}[ACCE] = ABC + \frac{8}{8}A$$


$$A + \frac{8}{8} + \frac{7}{6} + \frac{8}{8}A = \frac{7}{8} + \frac{8}{6} + \frac{7}{6}$$

Las expresiones algebraicas se redujeron con ayuda del álgebra de Boole

Map

Map Layout

Salida E-O:

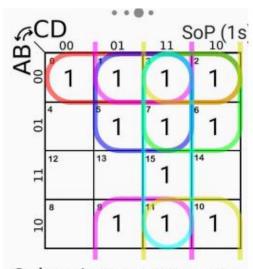

Seleccionar respuesta

$$S = \overline{A}\overline{B} + \overline{A}D + \overline{B}D + \overline{A}C + \overline{B}C + \overline{C}D$$

Groups

(0,1,2,3)	$\overline{A}.\overline{B}$
(1,3,5,7)	Ā.D
(1,3,9,11)	B.D
(2,3,6,7)	Ā.C
(2,3,10,11)	B.C
(3,7,11,15)	C.D

$$y = A'B' + A'D + B'D + A'C + B'C + CD$$

TABLA DE VERDAD


Α	В	С	D	SI=E-O	S2=N-S
0	0	0	0	I	0
0	0	0	I	I	0
0	0	1	0	I	0
0	0	- 1	ı	I	0
0	1	0	0	0	I
0	I	0	I	I	0
0	- 1	- 1	0	I	0
0	- 1	- 1	ı	l l	0
1	0	0	0	0	I
I	0	0	I	I	0
I	0	1	0	I	0
- 1	0	- 1	ı	I	0
I	1	0	0	0	I
I	ı	0	ı	0	I
I	1	1	0	0	I
I	- 1	- 1	1	I	0

		Map		
	$\overline{C}.\overline{D}$	C.D	C.D	$C.\overline{D}$
$\overline{A}.\overline{B}$	0	0	0	0
\overline{A} .B	1	0	0	0
A.B	1	1	0	1
$A.\overline{B}$	1	0	0	0


Map Layout							
	$\overline{C}.\overline{D}$	C.D	C.D	$C.\overline{D}$			
$\overline{A}.\overline{B}$	0	1	3	2			
\overline{A} .B	4	5	7	6			
A.B	12	13	15	14			
$A.\overline{B}$	8	9	11	10			

Seleccionar respuesta $S = B\overline{C}\overline{D} + A\overline{C}\overline{D} + AB\overline{C} + AB\overline{D}$

SALIDA N-S:

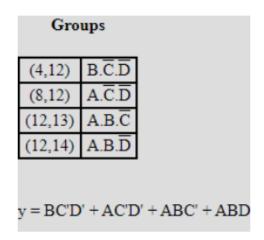


W	Х	Υ	Z	SI=E-O
0	0	0	0	0
0	0	0	1	0
0	0	ı	0	I
0	0	I	I	0
0	1	0	0	0
0	I	0	I	I
0	- 1	- 1	0	0
0		- 1		l l
ı	0	0	0	I
ı	0	0	ı	0
ı	0	- 1	0	0
I	0	1		I
ı	I	0	0	0
- 1	1	0	1	0
1	- 1	- 1	0	I
I	I	I	I	l

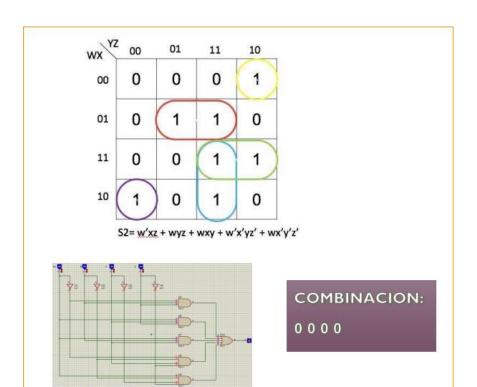

No	Α	В	С	D	Е	F
0	0	0	0	0	0	0
1	0	0	0	0	1	0
2	0	0	0	1	0	1
3	0	0	0	1	1	1
4	0	0	1	0	0	1
5	0	0	1	0	1	1
6	0	0	1	1	0	0
7	0	0	1	1	1	1
8	0	1	0	0	0	1
9	0	1	0	0	1	0
10	0	1	0	1	0	0
11	0	1	0	1	1	1
12	0	1	1	0	0	1
13	0	1	1	0	1	1
14	0	1	1	1	0	0
15	0	1	1	1	1	0
16	1	0	0	0	0	1
17	1	0	0	0	1	1
18	1	0	0	1	0	0
19	1	0	0	1	1	1
20	1	0	1	0	0	1
21	1	0	1	0	1	0
22	1	0	1	1	0	0
23	1	0	1	1	1	1

24	1	1	0	0	0	1
25	1	1	0	0	1	0
26	1	1	0	1	0	0
27	1	1	0	1	1	0
28	1	1	1	0	0	1
29	1	1	1	0	1	1
30	1	1	1	1	0	0
31	1	1	1	1	1	1

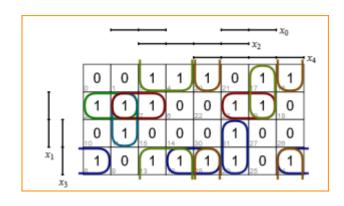

MAPA DE KARNAUGH

	Мар								
	$\overline{D}.\overline{E}$	D.E	D.E	$D.\overline{\overline{E}}$					
$\overline{A}.\overline{B}.\overline{C}$	0	0	1	1					
Ā.B.C	1	1	1	0					
A.B.C	1	1	0	0					
Ā.B.C	1	0	1	0					
A.B.C	1	1	1	0					
A.B.C	1	0	1	0					
A.B.C	1	1	1	0					
A.B.C	1	0	0	0					

Map Layout							
	D.E	D.E	D.E	D.Ē			
$\overline{A}.\overline{B}.\overline{C}$	0	1	3	2			
$\overline{A}.\overline{B}.C$	4	5	7	6			
A.B.C	12	13	15	14			
$\overline{A}.B.\overline{C}$	8	9	11	10			
A.B.C	16	17	19	18			
A.B.C	20	21	23	22			
A.B.C	28	29	31	30			
$A.B.\overline{C}$	24	25	27	26			

Groups

(4,12,20,28)	C.D.E
(3,7,19,23)	B.D.E
(8,12,24,28)	B.D.E
(4,5,12,13)	Ā.C.D
(2,3)	Ā.B.C.D
(29,31)	A.B.C.E
(3,11)	ĀČDE
(16,17)	A.B.C.D

y = CD'E' + B'DE + BD'E' + A'CD' + A'B'C'D + ABCE + A'C'DE + AB'C'D'

No.	Α	В	С	D	E	Z
0	0	0	0	0	0	1
- 1	0	0	0	0	1	0
2	0	0	0	1	0	1
3	0	0	0	- 1	- 1	0

4	0	0	- 1	0	0	- 1
5	0	0	- 1	0	- 1	0
6	0	0	- 1	1	0	1
7	0	0	- 1	1	- 1	0
8	0	- 1	0	0	0	1
9	0	- 1	0	0	- 1	0
10	0	1	0	1	0	X
Ш	0	- 1	0	- 1	- 1	X
12	0	- 1	- 1	0	0	x
13	0	- 1	- 1	0	- 1	X
14	0	- 1	- 1	1	0	x
15	0	- 1	- 1	- 1	- 1	X
16	-1	0	0	0	0	0
17	- 1	0	0	0	- 1	0
18	- 1	0	0	1	0	0
19	- 1	0	0	- 1	- 1	- 1
20	-1	0	- 1	0	0	0
21	1	0	- 1	0	- 1	0
22	- 1	0	- 1	1	0	- 1
23	- 1	0	- 1	- 1	- 1	0
24	- 1	- 1	0	0	0	0
25	- 1	- 1	0	0	- 1	- 1
26	- 1	1	0	1	0	X
27	- 1	- 1	0	- 1	- 1	X

28	1	- 1	- 1	0	0	х
29	1	1	- 1	0	1	X
30	1	1	- 1	1	0	X
31	- 1	- 1	- 1	1	- 1	X

MAPA DE KARNAUGH

	Map					
	$\overline{D}.\overline{E}$	D.E	D.E	D.Ē		
Ā.B.C	1	0	0	1		
A.B.C	1	0	0	1		
Ā.B.C	x	x	x	x		
Ā.B.C	1	0	x	x		
A.B.C	0	0	1	0		
A.B.C	0	0	0	1		
A.B.C	x	x	x	x		
A.B.C	0	1	x	x		

	Map Layout					
	$\overline{D}.\overline{E}$	D.E	D.E	D.Ē		
A.B.C	0	1	3	2		
A.B.C		5	7	6		
A.B.C	12	13	15	14		
A.B.C	8	9	11	10		
A.B.C	16	17	19	18		
A.B.C	20	21	23	22		
A.B.C	28	29	31	30		
A.B.C	24	25	27	26		

Groups 4,6,8,10,12,14)

(0,2,4,6,8,10,12,14)	Ā.Ē
(6,14,22,30)	C.D.Ē
(25,27,29,31)	A.B.E
(19,27)	A.C.D.E

y = A'E' + CDE' + ABE + AC'DE

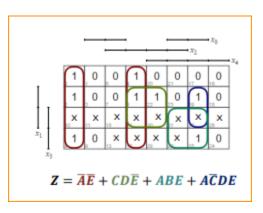


TABLA DE VERDAD

No.	A	В	С	D	Z
0	0	0	0	0	0
- 1	0	0	0	- 1	- 1
2	0	0	- 1	0	1
3	0	0	- 1	- 1	0
4	0	- 1	0	0	- 1
5	0	1	0	1	0
6	0	1	1	0	0
7	0	- 1	1	- 1	0
8	1	0	0	0	1
9	I	0	0	- 1	0

10	1	0	- 1	0	x
- 11	1	0	- 1	- 1	X
12	- 1	- 1	0	0	X
13	1	- 1	0	- 1	X
14	1	1	1	0	X
15	1	- 1	- 1	- 1	X


Map

Map Layout

Groups

(8,10,12,14)	A.D
(2,10)	B.C.D
(4,12)	B.C.D
(1)	A.B.C.D

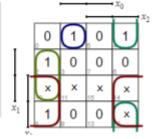 $\mathbf{y} = \mathbf{A}\mathbf{D}' + \mathbf{B}'\mathbf{C}\mathbf{D}' + \mathbf{B}\mathbf{C}'\mathbf{D}' + \mathbf{A}'\mathbf{B}'\mathbf{C}'\mathbf{D}$



 $z = A\overline{D} + \overline{B}C\overline{D} + B\overline{C}\overline{D} + \overline{A}\overline{B}\overline{C}D$